

EECS 16B Section 1B

W-1/20

Main Topic: Intro + 16A Review

Administrivia:

- Who am I?
- Overview of EECS 16B
- Questions?

Agenda:

• Circuit Relationships

- $V = IR$
- KCL / KVL
- Q1: KVL / KCL Review

• Op-Amps

- Golden Rules
- Q2: Op-Amp Summer

• Capacitors

- $Q = CV$
- $I_c(t) = C \frac{d}{dt} v_c(t)$
- Q3: Current Sources and Capacitors

• OPTIONAL - Q4: Linear Algebra Review

- Eigenvalues, span, nullspace

Recapping Resistors

Units:

Voltage (V, v)

Unit = Volts V


Current (I, i)

Unit = Amperes A

Resistance (R)

Unit = Ohms Ω

Resistors:

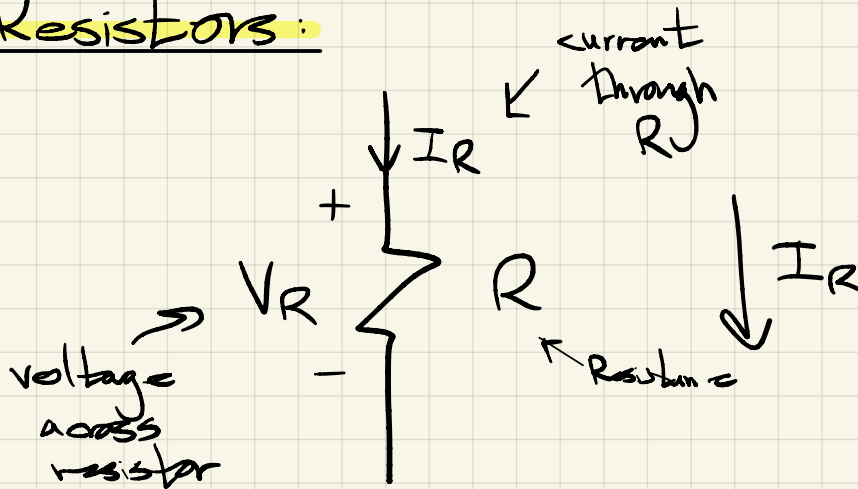

$$V = IR$$

$$R = \frac{V}{I}$$

$$I = \frac{V}{R}$$


Combining Resistors:

In Series:



$$R_{eq} = R_1 + R_2$$
$$= \sum R_i$$

In Parallel:

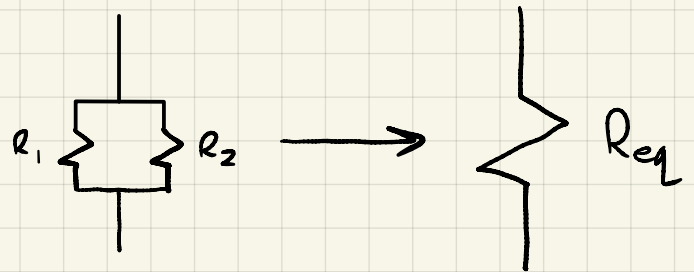

$$R_{eq} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$
$$= \frac{\text{"Product"}}{\text{"Sum"}} = \frac{\text{"x"}}{\text{"+"}}$$

1 KVL/KCL Review

Kirchhoff's Circuit Laws are two important laws used for analyzing circuits. Kirchhoff's Current Law (KCL) says that the sum of all currents entering a node must equal 0. For example, in Figure 1, the sum of all currents entering node 1 is $I_1 - I_2 - I_3 = 0$. Assuming that I_1 and I_3 are known, we can easily obtain a solvable equation for V_x by applying Ohm's law: $I_1 - \frac{V_x}{R_1} - I_3 = 0$.

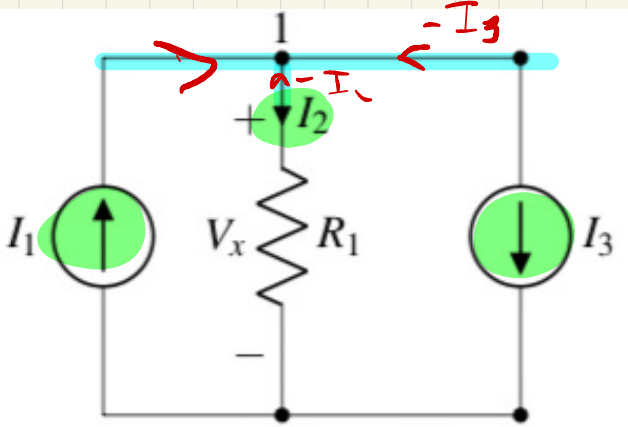


Figure 1: KCL Circuit

$$V_x = I_2 R_1$$

$$I_2 = \frac{V_x}{R_1}$$

$$\sum I_{in} = 0 \quad \sum I_{out} = 0$$

$$I_1 = I_2 + I_3$$

$$I_1 - I_2 - I_3 = 0$$

= "Glue together" components

Kirchhoff's Voltage Law (KVL) states that the **sum of all voltages in a circuit loop must equal 0**. To apply KVL to the circuit shown in Figure 2, we can add up voltages in the loop in the counterclockwise direction, which yields $-V_1 + V_x + V_y = 0$. Using the relationships $V_x = i \cdot R_1$ and $i = I_1$, we can solve for all unknowns in this circuit. You can use these two laws to solve any circuit that is planar and linear.

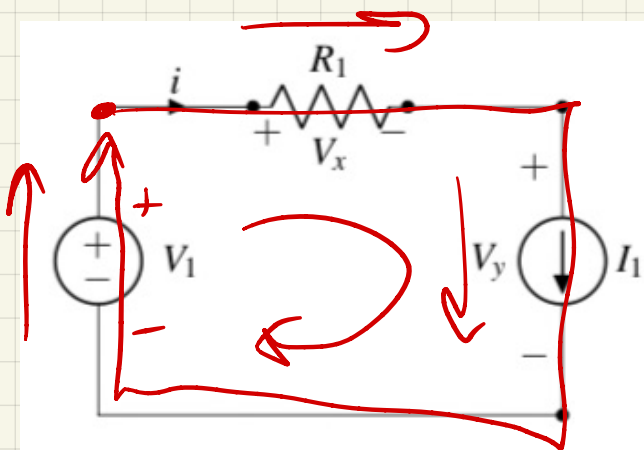


Figure 2: KVL Circuit

$$\sum V_{loop} = 0$$

+ \rightarrow - : drop, negative
 - \rightarrow + : rise, positive

$$-V_1 + V_y + V_x = 0$$

$$-V_x - V_y + V_1 = 0$$

1. KVL/KCL Review

Use Kirchhoff's Laws on the circuit below to find V_x in terms of V_{in}, R_1, R_2, R_3 .

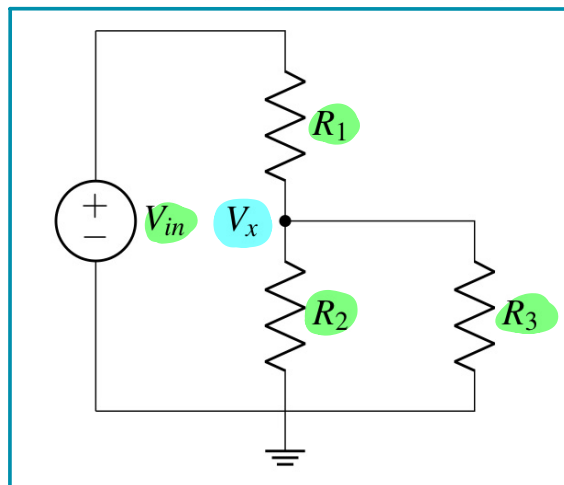


Figure 5: Example Circuit

$KCL: \sum I_{in} = 0$
 $\sum I_{out} = 0$
 $KVL: \sum V_{loop} = 0$
 $V = IR$
 $V^+ - V^- = IR$

- (a) What is V_x ?
- (b) As $R_3 \rightarrow \infty$, what is V_x ? What is the name we used for this type of circuit?

a) $IR_1 = IR_2 + IR_3$

$R_1: V_{R_1} = IR_1 R_1$


$V_{in} - V_x = IR_1 R_1$

$\frac{V_{in} - V_x}{R_1} = IR_1$

$R_2: V_{R_2} = IR_2 R_2$

$V_x = IR_2 R_2$

$R_3: V_x = IR_3 R_3$

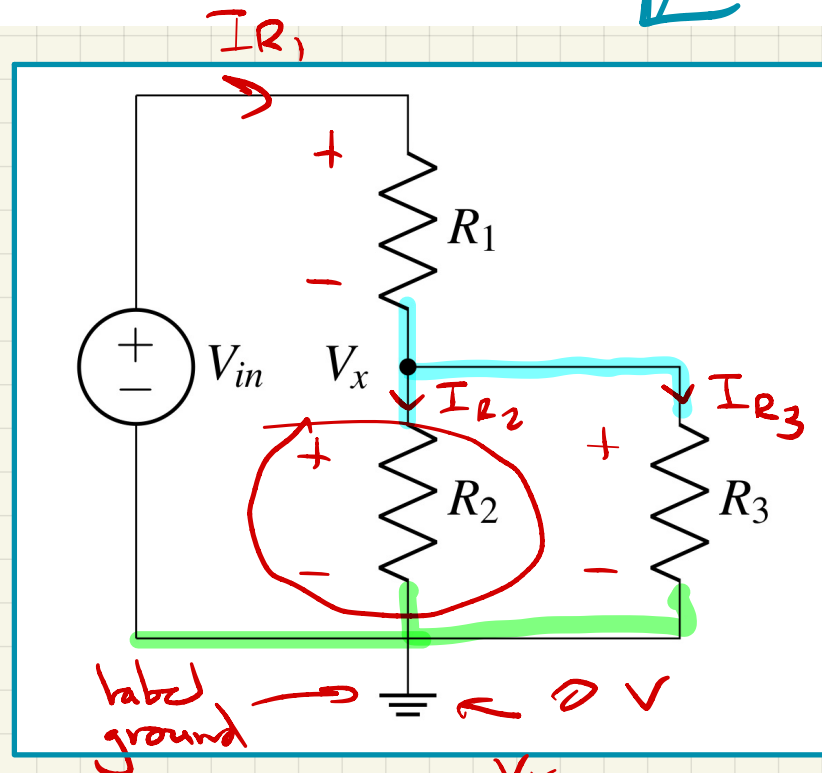

$IR_2 = \frac{V_x}{R_2}$

$IR_3 = \frac{V_x}{R_3}$

$\frac{V_{in} - V_x}{R_1} = \frac{V_x}{R_2} + \frac{V_x}{R_3}$

$V_x = V_{in} \frac{R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$

$R_2 R_3 (V_{in} - V_x) = R_1 R_3 V_x + R_1 R_2 V_x$

$$\underbrace{\left(\frac{V_{in} - V_x}{R_1} \right)}_{R_2 R_3} = \underbrace{\frac{V_x}{R_2}}_{R_1 R_3} + \underbrace{\frac{V_x}{R_3}}_{R_1 R_2} \quad R_1 R_2 R_3$$

$$R_2 R_3 (V_{in} - V_x) = R_1 R_3 V_x + R_1 R_2 V_x$$

$$R_2 R_3 V_{in} - \underline{R_2 R_3 V_x} = \quad \quad \quad "$$

$$R_2 R_3 V_{in} = R_1 R_3 \underline{V_x} + R_1 R_2 \underline{V_x} + R_2 R_3 \underline{V_x}$$

$$R_2 R_3 V_{in} = V_x \underline{\underline{(R_1 R_2 + R_1 R_3 + R_2 R_3)}}$$



$V_x = V_{in} \frac{R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3}$
--

⑥ "What if $R_3 \rightarrow \infty$?"

Method 1: Calculus

$$\begin{aligned}\lim_{R_3 \rightarrow \infty} V_x &= \lim_{R_3 \rightarrow \infty} V_{in} \frac{R_2 R_3}{R_1 R_2 + R_1 R_3 + R_2 R_3} \\ &= V_{in} \frac{R_2 R_3}{R_1 R_3 + R_2 R_3} \\ V_x &= V_{in} \frac{R_2}{R_1 + R_2}\end{aligned}$$

Method 2: Physics

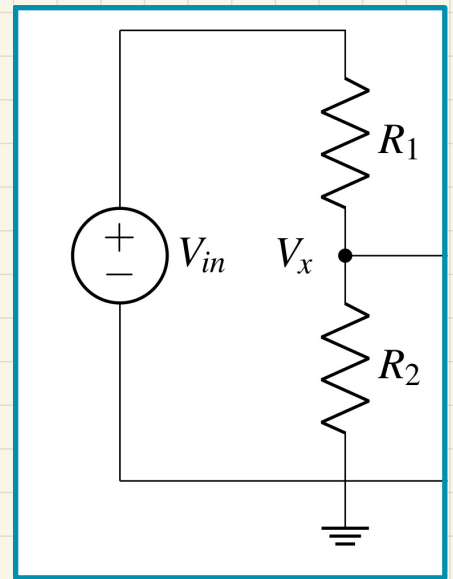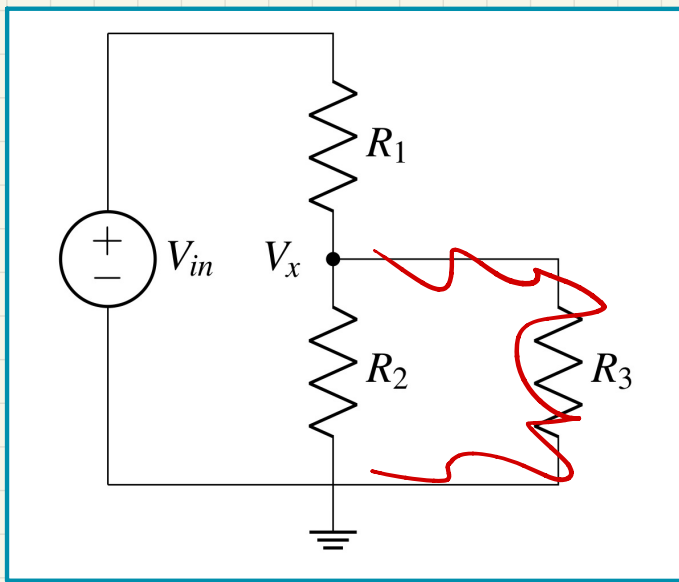

$R_3 \rightarrow \infty$, "Air", "open circuit"

2 Op-amp Review

Figure 3 shows the equivalent model of an op-amp. It is important to note that this is the general model of an op-amp, so our op-amp golden rules cannot be applied to this unless certain conditions are met.

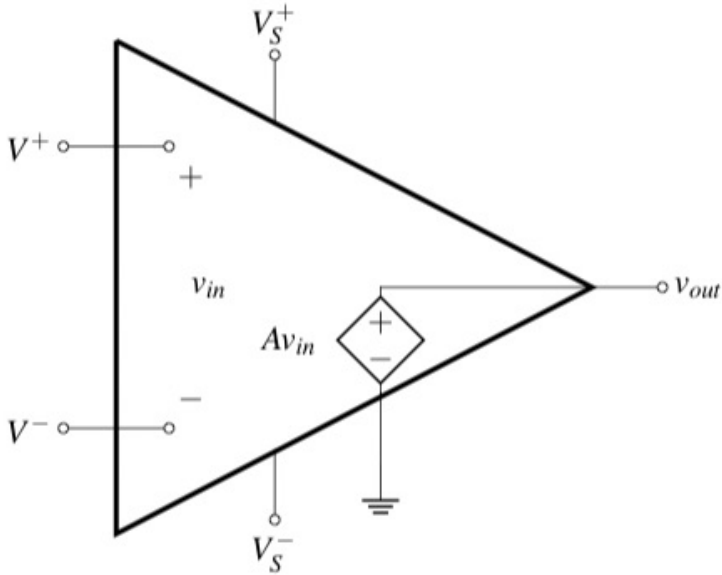


Figure 3: General Op-Amp Model

Conditions Required for the Golden Rules:

(a) $R_{in} \rightarrow \infty$

(b) $R_{out} \rightarrow 0$

(c) $A \rightarrow \infty$

(d) The op-amp must be operated in negative feedback.

When conditions (a)-(c) are met, the op-amp is considered ideal. Figure 4 shows an ideal op-amp in negative feedback, which can be analyzed using the Golden Rules.

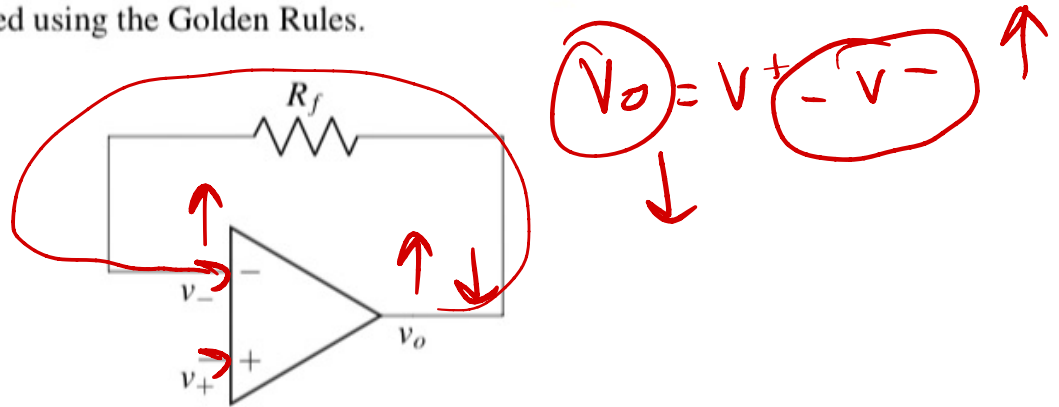


Figure 4: Ideal Op-Amp in Negative Feedback

Golden Rules of ideal op-amps in negative feedback:

(a) No current can flow into the input terminals ($I_- = 0$ and $I_+ = 0$).

(b) The (+) and (-) terminals are at the same voltage ($V_+ = V_-$).

$$V^+ = V^-$$

If you would like to review these concepts more in-depth, you can check out [op-amp introduction](#) and [op-amp negative feedback](#) from the EECS16A course notes.

2. Op-Amp Summer

Consider the following circuit (assume the op-amp is ideal):

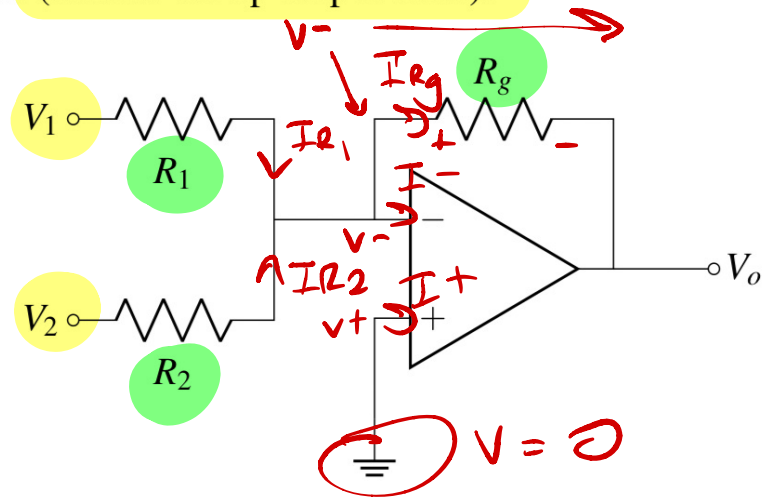


Figure 6: Op-amp Summer

What is the output V_o in terms of V_1 and V_2 ? You may assume that R_1 , R_2 , and R_g are known.

NFB? Yes. $\rightarrow v^- = v^+$
 $\rightarrow I^- = I^+ = 0$

$$I_{R_1} + I_{R_2} = I_{R_g} + I$$

$$V = IR$$

$$I = \frac{V}{R}$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = \frac{0 - V_o}{R_g}$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = -\frac{V_o}{R_g}$$

$$V_o = -\frac{R_g}{R_1} V_1 - \frac{R_g}{R_2} V_2$$

Capacitors

Q
↑
Charge
(Coulombs, C)

=

C
↑
Capacitance
(Farads, F)

V
↑
Voltage

$I_c \downarrow$ $\frac{C}{T}$ V_c

$$\frac{d}{dt} Q = I$$

$$\frac{d}{dt} (Q = CV)$$


$$I_c = C \frac{d}{dt} V_c$$

3. Current Sources And Capacitors (The following problem has been adapted from EECS16A Fall 20 Disc 9A.)

Recall charge has units of Coulombs (C), and capacitance is measured in Farads (F) = $\frac{\text{Coulomb}}{\text{Volt}}$.

It may also help to note metric prefix examples: $3\mu\text{F} = 3 \times 10^{-6}\text{F}$.

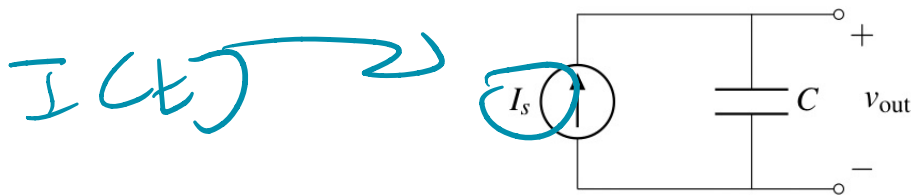Given the circuit below, find an expression for $v_{\text{out}}(t)$ in terms of I_s , C , V_0 , and t , where V_0 is the initial voltage across the capacitor at $t = 0$.



$$I_s = C \frac{d}{dt} v_{\text{out}}$$
$$\frac{I_s}{C} = \frac{d}{dt} v_{\text{out}}$$


Then plot the function $v_{\text{out}}(t)$ over time on the graph below for the following conditions detailed below. Use the values $I_s = 1\text{mA}$ and $C = 2\mu\text{F}$.

- (a) Capacitor is initially uncharged $V_0 = 0$ at $t = 0$.
- (b) Capacitor has been charged with $V_0 = +1.5\text{V}$ at $t = 0$.
- (c) **Practice:** Swap this capacitor for one with half the capacitance $C = 1\mu\text{F}$, which is initially uncharged $V_0 = 0$ at $t = 0$.

HINT: Recall the calculus identity $\int_a^b f'(x)dx = f(b) - f(a)$, where $f'(x) = \frac{df}{dx}$.

a

b

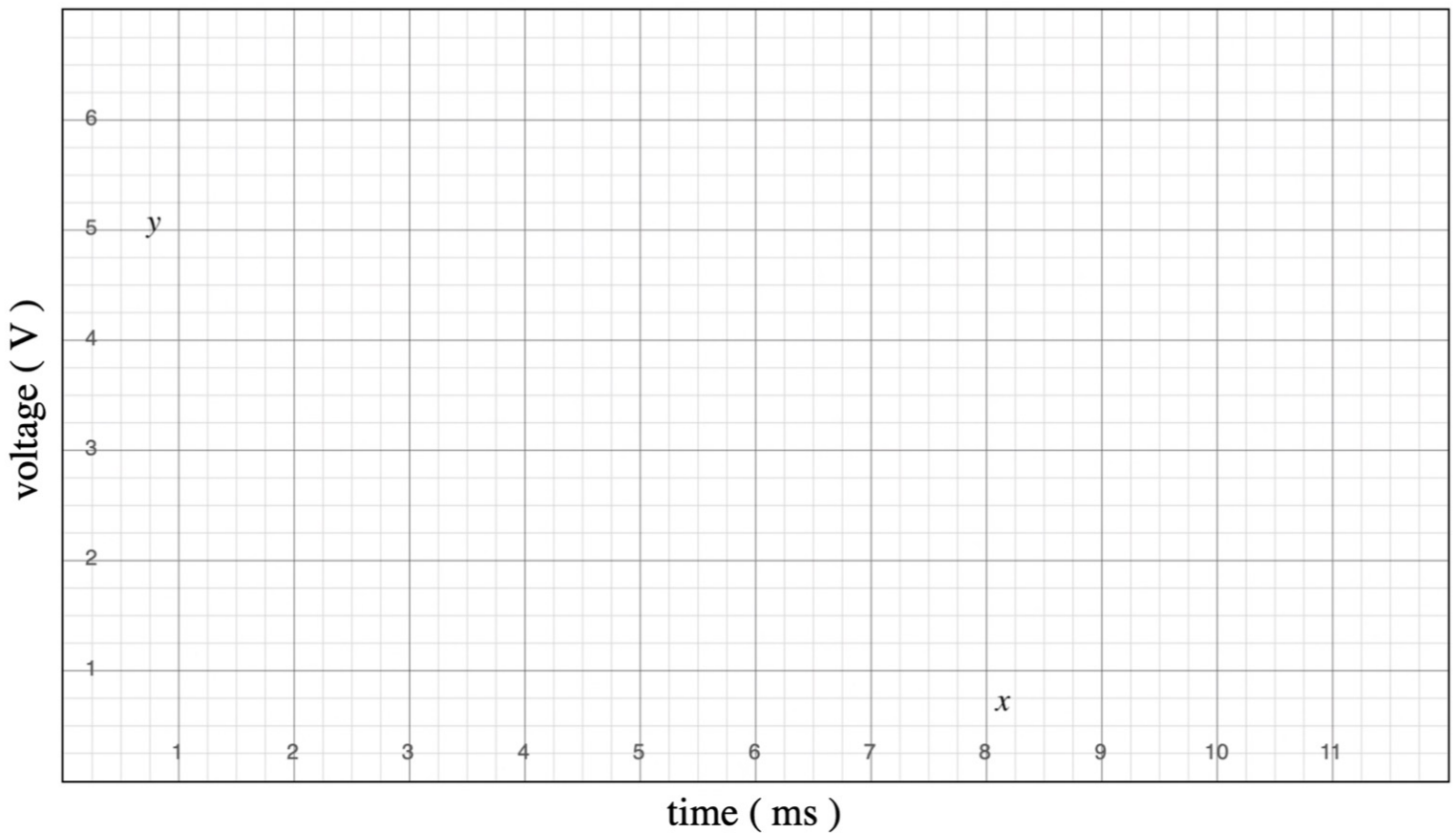

4. Linear Algebra Review

For the following matrices, find the following properties:

- i. What is the column space of the matrix?
- ii. What is the null space of the matrix?
- iii. What are the eigenvalues and corresponding eigenspaces for the matrix?

(a) $\begin{bmatrix} 2 & 4 \\ 0 & 3 \end{bmatrix}$

(b) $\begin{bmatrix} 1 & -2 \\ 2 & -4 \end{bmatrix}$

(c) $\begin{bmatrix} 2 & 0 & 0 \\ 0 & 0.5 & 0.5 \\ 0 & 0.5 & 0.5 \end{bmatrix}$

For this matrix you are told that the eigenvalues are: 2, 1, and 0.